

Multicycle Processor

412 Final Project

Aaron Donawerth, Kevin Phan, Lucas Magasweran

5/4/2011

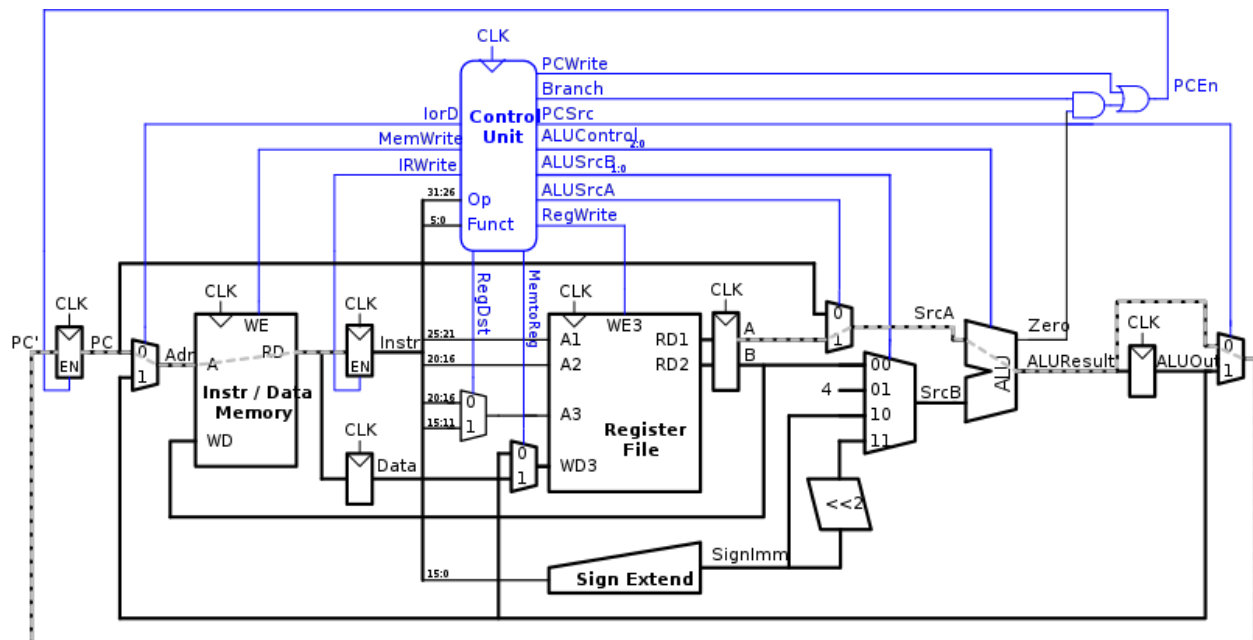


Table of Contents

Multicycle Implementation.....	3
Multicycle Datapath	4
R-Type.....	6
I-Type.....	6
J-Type.....	7
Performance Analysis	8
Conclusion.....	11
Verilog.....	12
mipstest.v.....	12
topmulti.v.....	13
mipsmulti.v	13
mipsparts.v.....	18
mipsmem.v.....	20
Mipstest.asm.....	20
Simulation	23
Bibliography	24
Reference of Images.....	25

Multicycle Implementation

The multicycle implementation fixes many of the shortcomings of the single cycle design. The single cycle processor must have a clock period long enough to support the slowest instruction. However the multicycle is not hampered by this limitation. With multicycle, multiple clock cycles with shorter periods are used. Economy of hardware is another weakness of single cycle implementations. Multicycle implementation reuses components of the datapath, making it more cost efficient.

Multiple clock cycles allow the processor to break up an instruction into shorter steps. With multicycle, a subset of actions required for an instruction is performed in one cycle. As a result, shorter instructions are executed faster. This process is analogous to a dental office allotting time to patients in multiples of 15 minutes, depending on the amount of work that is anticipated¹. Figure 1 illustrates the single cycle and multicycle clock periods and how clock period affects instruction execution.

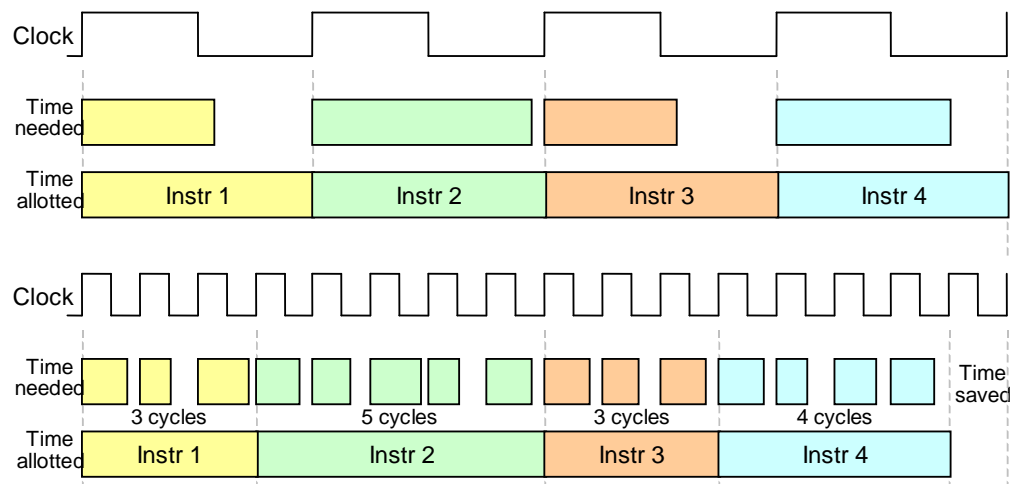


Figure 1: Multicycle vs Single Cycle

¹ Parhami, Behrooz. Computer Architecture, New York: Oxford University Press, 2005

The economy of hardware is improved by reusing or combining components. The single cycle uses three adders (two for PC logic and one ALU) and separate memory for data and instructions. The multicycle implementation combines the data and instruction memory and uses one ALU to execute all arithmetic tasks. The cost of production goes down because only one ALU needs to be built rather than several adders.

The design of the multicycle processor is similar to the single cycle. The multicycle processor consists of the datapath and controller block. A controller is added to produce different signals for different stages of execution. An external memory is connected to the processor. The instructions and data come from the external memory. The datapath is comprised of combinational logic units that connect architectural state elements. Non architectural state elements such as registers are used to hold intermediate results between stages.

Multicycle Datapath

The multicycle datapath builds upon the single cycle. The multicycle datapath has a PC register and a Register File similar to the single cycle datapath. Unlike the single cycle, the multicycle combines the data and instruction memories. Other components such as multiplexers, sign extenders, and ALU are included in the datapath. The full datapath is shown in the figure below.

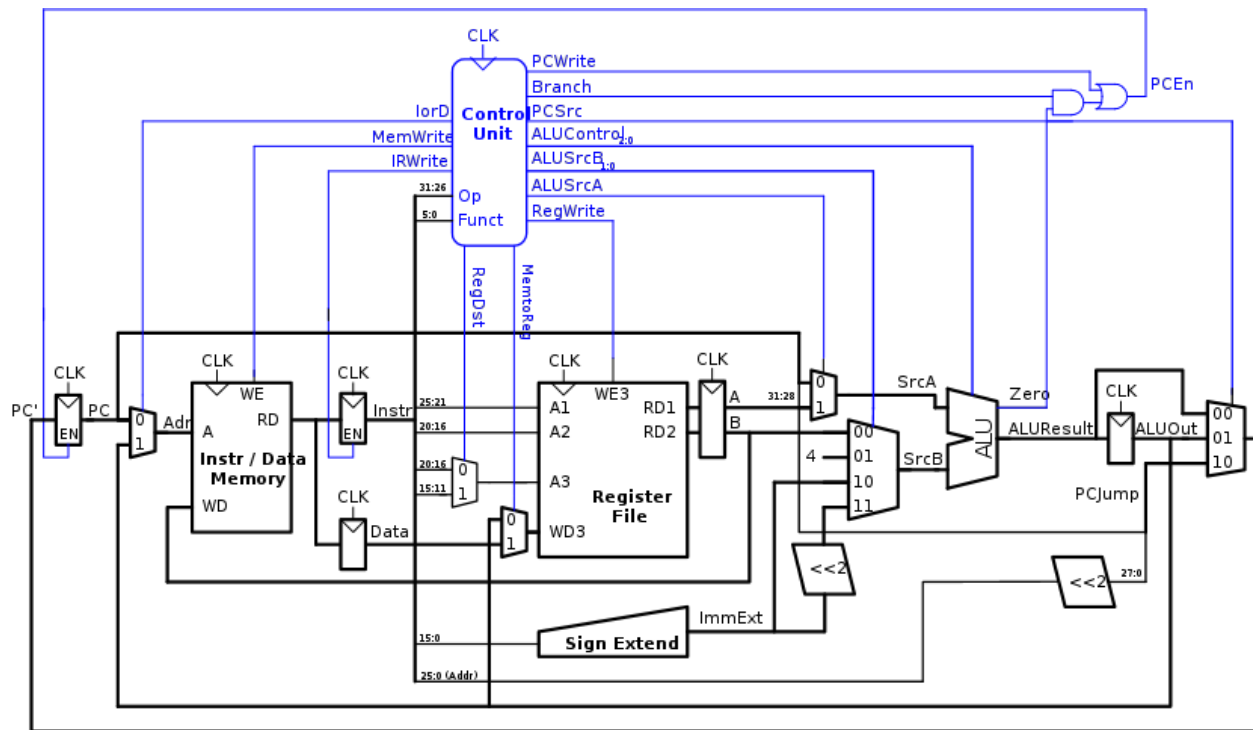


Figure 2: Multicycle Datapath

The multicycle datapath follows the five stage execution process: Fetch, decode, ALU, data access, and register write. Below are the control signals for the fetch and decode steps.

lrdD = 0
AluSrcA = 0
ALUSrcB = 01
ALUOp = 00
PCSrc = 0
IRWrite = 1
PCWrite = 1

Figure 3: Fetch Control Signals

ALUSrcA = 0
ALUSrcB = 11
ALUOp = 00

Figure 4: Decode Control Signals

The fetch control signals are used to calculate PC+4 for the next instruction. The decode control signals are mainly used for branching. After the fetch and decode steps, the datapath of I-type, J-type, and R-type instructions vary.

R-Type

If the opcode is a R type instruction, the result must be calculated using the ALU and stored back to the register. To carry out ALU calculation, ALUSrcA is set to 1, ALUSrcB is set to 0, and ALUOp is set to 10. ALUSrcA selects the \$rs register to be used as SrcA and ALUSrcB selects \$rt register to be used as SrcB of the ALU. ALUOp set to 10 indicates to the controller that ALU operation mode is dependent on the function field of the instruction. For result storage, RegDst and RegWrite are set to 1 and MemtoReg is set to 0. RegDst selects \$rd register as the write destination and MemtoReg indicates the data to be written is from ALU. RegWrite serves as a write enable for the Register File.

I-Type

Unlike the R type instruction, not all I-type instructions are carried out the same. The load word (lw), store word (sw), add immediate (addi), and branch if equal (beq) use different amounts of cycles. After the lw and sw instructions are decoded, the address for memory access must be computed by adding a base address located in the \$rs register and a sign extended immediate. Control signals must be set to control the multiplexers that handle inputs at various sections of the datapath. The appropriate control signals for this step are ALUSrcA to 1, ALUSrcB to 10, and ALUOp to 00. Next, the calculated address is used to access memory; lorD is set to 1 to indicate that the incoming address is from the ALU. For sw, MemWrite is set to 1. The data located in the WriteData (WD) portion is stored to memory. Register \$rt is always fed to WD, however the data from \$rt is not written to memory unless MemWrite is asserted. The sw instruction is done, but lw has to write back to the register. Three control signals are set: RegDst

to 0, MemtoReg to 1, and RegWrite to 1. Similar to the memory portion, if RegWrite is not set to 1, the data inside WD3 will not be written to the Register File.

For addi, \$rs is still added to a sign extended immediate, but instead of using the result to access memory, the result is stored in the address located in \$rt. The control signals for the ALU computation remain the same as the lw and sw instructions. Afterwards, the result is written to the Register File. The control signals for this are RegDst and RegWrite to 1 and MemtoReg to 0.

The beq instruction has less stages than all of the other I type instructions. The branch is evaluated immediately when the ALU result is calculated. To test if a branch is equal, the values stored in \$rs and \$rt are subtracted from each other. If the differences between the two registers are zero, the values are equal. The result of the subtraction is indicated by the zero signal from the ALU. Once the zero signal is set to one, the result is fed into a two input AND gate with the branch signal. The result of that AND gate will produce a 1 and make PCEn 1. While this takes place, the result of the ALU is fed into the PC. With PCEn set to 1, the value of PC will be overwritten with this result. The control signals needed to carry out the branch are ALUSrcA to 1, ALUSrcB to 00, ALUOp to 01, Branch to 1, and PCSrc to 1.

J-Type

Whenever a J-Type instruction is indicated by the opcode, the 26 least significant bits are taken from the instruction and modified as a pseudo direct address. After the instruction is decoded, the PCSrc control signal is set to 10 and the PCWrite to 1. The PCSrc signal allows the ALUResult to circumvent the register and go directly to the PC. The PCWrite makes the OR gate of PCEn to produce a 1 and enable the PC register to be overwritten.

To further understand how these datapaths are linked together, a state diagram of the Finite State Machine (FSM) is used. The state diagram is also helpful in gauging the performance of the multicycle processor. The FSM is shown below.

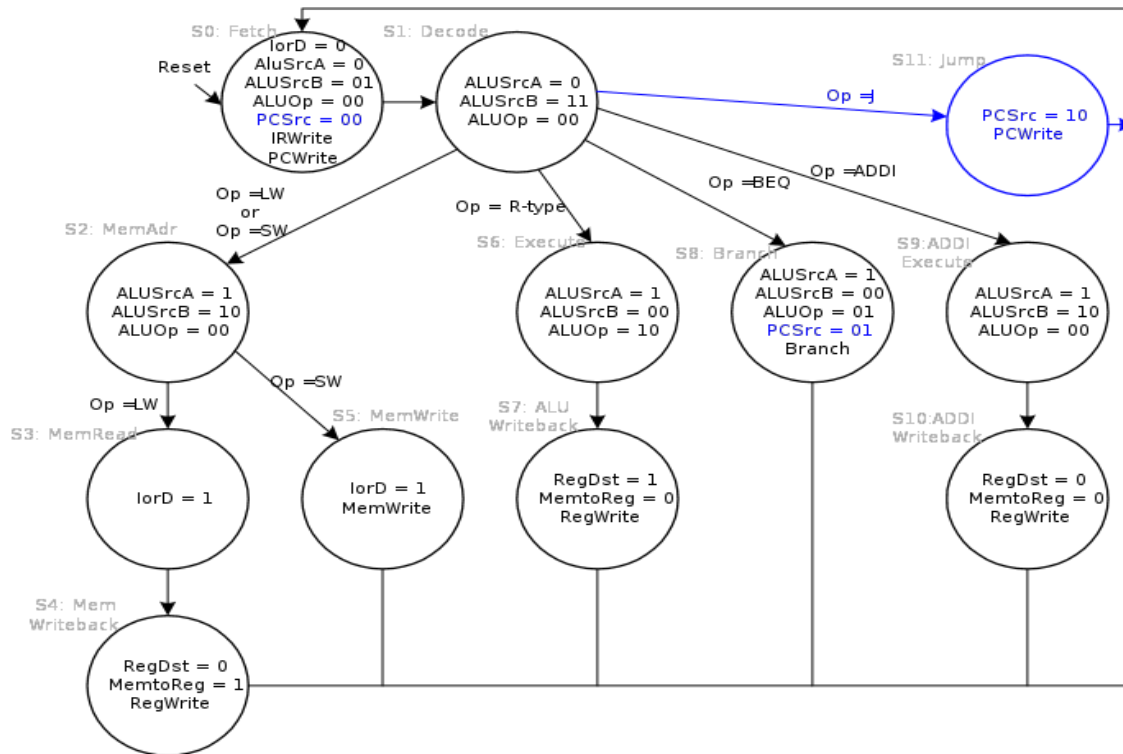


Figure 3: FSM of Multicycle

Performance Analysis

The number of cycles and cycle time determine the instruction execution time. Even though the single cycle only uses one cycle, the multicycle does less work per cycle. The number of cycles per multicycle instruction is equivalent to the number of stages per instruction. Below is the number of cycles needed for each instruction.

Load Word = 5 Cycles
Store Word = 4 Cycles
R-Type = 4 Cycles
Branch = 3 Cycles
Jump = 3 Cycles

Figure 5: Required Cycles for Instructions

The cycles per instruction (CPI) of the multicycle processor can be calculated by taking weighted averages of the types of instructions. The SPECINT2000 benchmark lists the instruction distribution as 25% loads, 10% stores, 11% branches, 2% jumps, and 52% R-type instructions.

Load	→	.25(5) = 1.25 CPI
Store	→	.1(4) = .4 CPI
Jump	→	.2(3) = .06 CPI
R-Type	→	.52(4) = 2.08 CPI
Branch	→	.11(3) = .33 CPI
Avg CPI		= 4.12 CPI

Figure6: CPI Calculation

The CPI of the multicycle is better than the worst case CPI of 5. The single cycle performance is hindered by the worst instruction. The CPI can be used to determine the MIPS of a processor and the execution time. The MIPS of a processor is calculated by dividing the frequency of the processor by its CPI. Execution time is calculated by the following equation.

$$\text{Execution Time} = (\# \text{ of instructions})(\text{CPI})(\text{Period})$$

The period (T_c) of the multicycle processor is based off of the critical paths of the datapath. The equation of the critical paths is shown below.

$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$

The delays of each circuit element are listed in the table below.

Element	Parameter	Delay(ps)
Register clock to Q	t_{pcq}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory Read	t_{mem}	250
Register File Read	t_{RFread}	150
Register File Setup	$t_{RFsetup}$	20

The number of instructions for our testbench is 16, which equates to 66 cycles. The amount of cycles is approximately equal to the average CPI multiplied number of instructions which is 65.92. Given the close proximity of these numbers, the average CPI will be used in the calculations. Using the values and the equations listed above with our testbench, the period and the execution time of the multicycle processor can be calculated.

$$325 \text{ ps} = 30 + 25 + 250 + 20$$

$$21.42 \text{ ns} = (16)(4.12)(325 \times 10^{-12})$$

Compared to the single cycle processor which has a cycle time of 950ps, a CPI, and an execution time of 95 seconds, the multicycle is slower². Single cycle is faster than the multicycle because every instruction is not the same length and the overhead from register clk-to-Q and setup is paid every step.

² Harris, David Money. Harris, Sarah L. Digital Design and Computer Architecture, San Francisco: Morgan Kaufman Publishers, 2007, Page 399

Conclusion

The major advantage of the multicycle processor is the economy. The ability to reuse and combine components makes multicycle an attractive option. Since multicycle is not limited by the slowest instruction, the execution time can be improved by increasing the clock rate. With an increased clock rate, the execution time drops. The multicycle processor is not the optimal processor. The pipeline processor strives to improve upon the single cycle and multicycle by increasing its execution time and by keeping the CPI down.

Verilog

mipstest.v

```
// HDL Example 7.12 MIPS TESTBENCH
// Test bench for MIPS processor

module testbench();

    reg    clk;
    reg    reset;

    wire [31:0] writedata, dataadr;
    wire memwrite;

    // keep track of execution status
    reg [31:0] cycle;

    // instantiate device to be tested
    topmulti dut(clk, reset, writedata, dataadr, memwrite);

    // initialize test
    initial
    begin
        reset <= 1; # 12; reset <= 0;
        cycle <= 1;
    end

    // generate clock to sequence tests
    always
    begin
        clk <= 1; # 5; clk <= 0; # 5;
        cycle <= cycle + 1;
    end

    // check results
    // If successful, it should write the value 7 to address 84
    always@(negedge clk)
    begin
        if (memwrite) begin
            if (dataadr === 84 & writedata == 7) begin
                $display("Simulation succeeded");
                $stop;
            end else if (dataadr !== 80) begin
                $display("Simulation failed");
                $stop;
            end
        end
    end
end
```

```

    end
endmodule

```

topmulti.v

```

// Top-level Module of a Multicycle MIPS processor
// From Exercise 7.22
module topmulti(input    clk, reset,
                output [31:0] writedata, adr,
                output    memwrite);

    wire [31:0] readdata;

    // instantiate processor and memory
    mips mips(clk, reset, adr, writedata, memwrite, readdata);
    mem mem(clk, memwrite, adr, writedata, readdata);

endmodule

```

mipsmulti.v

```

// Multicycle MIPS processor
module mips(input    clk, reset,
            output [31:0] adr, writedata,
            output    memwrite,
            input  [31:0] readdata);

    wire    zero, pcen, irwrite, regwrite,
            alusrca, iord, memtoreg, regdst;
    wire [1:0] alusrcb;
    wire [1:0] pcsrc;
    wire [2:0] alucontrol;
    wire [5:0] op, funct;

    // The control unit receives the current instruction from the datapath and tells the
    // datapath how to execute that instruction.
    controller c(clk, reset, op, funct, zero,
                pcen, memwrite, irwrite, regwrite,
                alusrca, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol);

    // The datapath operates on words of data. It
    // contains structures such as memories, registers, ALUs, and multiplexers.
    // MIPS is a 32-bit architecture, so we will use a 32-bit datapath.
    datapath dp(clk, reset,
                pcen, irwrite, regwrite,
                alusrca, iord, memtoreg, regdst,
                alusrcb, pcsrc, alucontrol,
                op, funct, zero,
                adr, writedata, readdata);

```

```

endmodule

// The main controller produces multiplexer select and register enable
// signals for the datapath. The select signals are MemtoReg, RegDst,
// IorD, PCSrc, ALUSrcB, and ALUSrcA. The enable signals are IRWrite,
// MemWrite, PCWrite, Branch, and RegWrite.
module controller(input  clk, reset,
                  input  [5:0] op, funct,
                  input    zero,
                  output   pcen, memwrite, irwrite, regwrite,
                  output   alusrcA, iord, memtoreg, regdst,
                  output [1:0] alusrcb,
                                     output [1:0] pcsrc,
                  output [2:0] alucontrol);

wire [1:0] aluop;
wire   branch, pcwrite;

// Main Decoder and ALU Decoder subunits.
maindec md(clk, reset, op,
            pcwrite, memwrite, irwrite, regwrite,
            alusrcA, branch, iord, memtoreg, regdst,
            alusrcb, pcsrc, aluop);
aludec ad(funct, aluop, alucontrol);

assign pcen = pcwrite | (branch & zero);

endmodule

// The controller receives the current instruction from the datapath
// and tell the datapath how to execute that instruction.
module maindec(input  clk, reset,
               input  [5:0] op,
               output   pcwrite, memwrite, irwrite, regwrite,
               output   alusrcA, branch, iord, memtoreg, regdst,
               output [1:0] alusrcb,
                                   output [1:0] pcsrc,
               output [1:0] aluop);

// FSM States
parameter  FETCH           = 5'b00000; // State 0
parameter  DECODE         = 5'b00001; // State 1
parameter  MEMADR         = 5'b00010;  // State 2
parameter  MEMRD          = 5'b00011;  // State 3
parameter  MEMWB          = 5'b00100;  // State 4
parameter  MEMWR          = 5'b00101;  // State 5
parameter  EXECUTE        = 5'b00110;  // State 6
parameter  ALUWRITEBACK   = 5'b00111;  // State 7

```

```

parameter BRANCH          = 5'b01000;    // State 8
parameter ADDIEXECUTE     = 5'b01001;    // State 9
parameter ADDIWRITEBACK   = 5'b01010;    // state a
parameter JUMP            = 5'b01011;    // State b

```

```
// MIPS Instruction Opcodes
```

```

parameter LW   = 6'b100011;    // load word lw
parameter SW   = 6'b101011;    // store word sw
parameter RTYPE = 6'b000000;    // R-type
parameter BEQ  = 6'b000100;    // branch if equal beq
parameter ADDI = 6'b001000;    // add immediate addi
parameter J    = 6'b000010;    // jump j

```

```
reg [4:0] state, nextstate;
```

```
reg [16:0] controls;
```

```
// state register
```

```
always @(posedge clk or posedge reset)
```

```
    if(reset) state <= FETCH;
```

```
    else state <= nextstate;
```

```
// next state logic
```

```
always @( * )
```

```
    case(state)
```

```
        FETCH: nextstate <= DECODE;
```

```
        DECODE: case(op)
```

```
            LW:    nextstate <= MEMADR;
```

```
            SW:    nextstate <= MEMADR;
```

```
            RTYPE: nextstate <= EXECUTE;
```

```
            BEQ:   nextstate <= BRANCH;
```

```
            ADDI:  nextstate <= ADDIEXECUTE;
```

```
            J:     nextstate <= JUMP;
```

```
            default: nextstate <= FETCH; // should never happen
```

```
        endcase
```

```
        MEMADR: case(op)
```

```
            LW:    nextstate <= MEMRD;
```

```
            SW:    nextstate <= MEMWR;
```

```
            default: nextstate <= FETCH; // should never happen
```

```
        endcase
```

```
        MEMRD: nextstate <= MEMWB;
```

```
        MEMWB: nextstate <= FETCH;
```

```
        MEMWR: nextstate <= FETCH;
```

```
        EXECUTE: nextstate <= ALUWRITEBACK;
```

```
        ALUWRITEBACK: nextstate <= FETCH;
```

```
        BRANCH: nextstate <= FETCH;
```

```
        ADDIEXECUTE: nextstate <= ADDIWRITEBACK;
```

```
        ADDIWRITEBACK: nextstate <= FETCH;
```

```
        JUMP: nextstate <= FETCH;
```

```

    default: nextstate <= FETCH; // should never happen
endcase

// output logic
assign {pcwrite, memwrite, irwrite, regwrite,
       alusrca, branch, iord, memtoreg, regdst,
       alusrcb, pcsrc,
       aluop} = controls;

always @( * )
case(state)
    FETCH:    controls <= 19'b1010_00000_0100_00;
    DECODE:   controls <= 19'b0000_00000_1100_00;
    MEMADR:   controls <= 19'b0000_10000_1000_00;
    MEMRD:    controls <= 19'b0000_00100_0000_00;
    MEMWB:    controls <= 19'b0001_00010_0000_00;
    MEMWR:    controls <= 19'b0100_00100_0000_00;
    EXECUTE:  controls <= 19'b0000_10000_0000_10;
    ALUWRITEBACK: controls <= 19'b0001_00001_0000_00;
    BRANCH:   controls <= 19'b0000_11000_0001_01;
    ADDIEXECUTE: controls <= 19'b0000_10000_1000_00;
    ADDIWRITEBACK: controls <= 19'b0001_00000_0000_00;
    JUMP:     controls <= 19'b1000_00000_0010_00;
    default:  controls <= 19'b0000_xxxxx_xxxx_xx; // should never happen
endcase
endmodule

module aludec(input  [5:0] funct,
              input  [1:0] aluop,
              output reg [2:0] alucontrol);

always @( * )
case(aluop)
    3'b000: alucontrol <= 3'b010; // add
    3'b001: alucontrol <= 3'b010; // sub
    // RTYPE instruction use the 6-bit funct field of instruction to specify ALU operation
    3'b010: case(funct)
        6'b100000: alucontrol <= 3'b010; // ADD
        6'b100010: alucontrol <= 3'b110; // SUB
        6'b100100: alucontrol <= 3'b000; // AND
        6'b100101: alucontrol <= 3'b001; // OR
        6'b101010: alucontrol <= 3'b111; // SLT
        default: alucontrol <= 3'bxxx; // ???
    endcase
    default: alucontrol <= 3'bxxx; // ???
endcase
endmodule

```



```

module datapath(input    clk, reset,
               input    pcen, irwrite, regwrite,
               input    alusrca, iord, memtoreg, regdst,
               input [1:0] alusrcb,
                                   input [1:0] pcsrc,
               input [2:0] alucontrol,
               output [5:0] op, funct,
               output    zero,
               output [31:0] adr, writedata,
               input [31:0] readdata);

// Internal signals of the datapath module

wire [4:0] writereg;
wire [31:0] pcnext, pc;
wire [31:0] instr, data, srca, srcb;
wire [31:0] a;
wire [31:0] alurest, aluout;
wire [31:0] signimm; // the sign-extended immediate
wire [31:0] signimmsh; // the sign-extended immediate shifted left by 2
wire [31:0] wd3, rd1, rd2;

// op and funct fields to controller
assign op = instr[31:26];
assign funct = instr[5:0];

// datapath
flopnr #(32) pcreg(clk, reset, pcen, pcnext, pc);
mux2  #(32) adrmux(pc, aluout, iord, adr);
flopnr #(32) instrreg(clk, reset, irwrite, readdata, instr);
flop  #(32) datareg(clk, reset, readdata, data);

mux2  #(5) regdstmux(instr[20:16], instr[15:11], regdst, writereg);
mux2  #(32) wdmux(aluout, data, memtoreg, wd3);
regfile rf(clk, regwrite, instr[25:21], instr[20:16],
           writereg, wd3, rd1, rd2);
signext se(instr[15:0], signimm);
sl2     immsh(signimm, signimmsh);
flopnr #(32) areg(clk, reset, rd1, a);
flopnr #(32) breg(clk, reset, rd2, writedata);
mux2  #(32) srcamux(pc, a, alusrca, srca);
mux4  #(32) srcbmux(writedata, 32'b100, signimm, signimmsh,
                   alusrcb, srcb);
alu    alu(srca, srcb, alucontrol,
           alurest, zero);
flopnr #(32) alureg(clk, reset, alurest, aluout);
mux3  #(32) pcmux(alurest, aluout,
                 {pc[31:28], instr[25:0], 2'b00}, pcsrc, pcnext);

```

```
endmodule
```

mipsparts.v

```
// 32-bit ALU
// Function codes are defined on page 243
module alu(    input [31:0] A, B,
              input [2:0] F,
              output reg [31:0] Y, output Zero);

    always @ ( * )
        case (F[2:0])
            3'b000: Y <= A & B;
            3'b001: Y <= A | B;
            3'b010: Y <= A + B;
            //3'b011: Y <= 0; // not used
            3'b011: Y <= A & ~B;
            3'b101: Y <= A + ~B;
            3'b110: Y <= A - B;
            3'b111: Y <= A < B ? 1:0;
            default: Y <= 0; //default to 0, should not happen
        endcase

    assign Zero = (Y == 32'b0);
endmodule

// Example 7.6 Register file
module regfile(input    clk,
              input    we3,
              input [4:0] ra1, ra2, wa3,
              input [31:0] wd3,
              output [31:0] rd1, rd2);

    reg [31:0] rf[31:0];

    // three ported register file
    // read two ports combinationaly
    // write third port on rising edge of clock
    // register 0 hardwired to 0

    always @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule
```

// Example 7.8 Left Shift (Multiply by 4)

```
module sl2(input [31:0] a,
          output [31:0] y);
```

```
    // shift left by 2
    assign y = {a[29:0], 2'b00};
endmodule
```

// Example 7.9 Sign Extension

```
module signext(input [15:0] a,
               output [31:0] y);
```

```
    assign y = {{16{a[15]}}, a};
endmodule
```

// Example 7.10 Resettable Flip-flop with width parameter

```
module flopr #(parameter WIDTH = 8)
    (input      clk, reset,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
```

```
    always @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule
```

// Example 4.20 RESETTABLE ENABLED REGISTER with width parameter

```
module flopenr #(parameter WIDTH = 8)
    (input      clk, reset,
     input      en,
     input  [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
```

```
    always @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule
```

// Example 4.5 2:1 MULTIPLEXER with width parameter

```
module mux2 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1,
     input      s,
     output [WIDTH-1:0] y);
```

```
    assign y = s ? d1 : d0;
endmodule
```

// 3:1 MULTIPLEXER with width parameter

```

module mux3 #(parameter WIDTH = 8)
    (input  [WIDTH-1:0] d0, d1, d2,
     input  [1:0]      s,
     output [WIDTH-1:0] y);

    assign #1 y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

// Example 4.6 4:1 MULTIPLEXER with width parameter
module mux4 #(parameter WIDTH = 8)
    (input  [WIDTH-1:0] d0, d1, d2, d3,
     input  [1:0]      s,
     output reg [WIDTH-1:0] y);

    always @( * )
        case(s)
            2'b00: y <= d0;
            2'b01: y <= d1;
            2'b10: y <= d2;
            2'b11: y <= d3;
        endcase
endmodule

```

mipsmem.v

```

// Multicycle MIPS instruction and data memory
// "memfile.dat" contains a test program
module mem(input      clk, we,
           input  [31:0] a, wd,
           output [31:0] rd);

    reg [31:0] RAM[63:0];

    initial
        begin
            $readmemh("memfile.dat",RAM);
        end

    assign rd = RAM[a[31:2]]; // word aligned

    always @(posedge clk)
        if (we)
            RAM[a[31:2]] <= wd;
Endmodule

```

Mipstest.asm

```

main:  addi $2, $0,      # initialize $2 = 5 0      20020005
       addi $3, $0, 12  # initialize $3 = 12 4      2003000c

```

```

addi $7, $3, -9 # initialize $7 = 3 - 8 2067fff7
or $4, $7, $2 # $4 <= 3 or 5 = 7 c 00e22025
and $5, $3, $4 # $5 <= 12 and 7 = 4 10 00642824
add $5, $5, $4 # $5 = 4 + 7 = 11 14 00a42820
beq $5, $7, end # shouldn't be taken 18 10a7000a
slt $4, $3, $4 # $4 = 12 < 7 = 0 1c 0064202a
beq $4, $0, around # should be taken 20 10800001
addi $5, $0, 0 # shouldn't happen 24 20050000
around: slt $4, $7, $2 # $4 = 3 < 5 = 1 28 00e2202a
add $7, $4, $5 # $7 = 1 + 11 = 12 2c 00853820
sub $7, $7, $2 # $7 = 12 - 5 = 7 30 00e23822
sw $7, 68($3) # [80] = 7 34 ac670044
lw $2, 80($0) # $2 = [80] = 7 38 8c020050
j end # should be taken 3c 08000011
addi $2, $0, 1 # shouldn't happen 40 20020001
end: sw $2, 84($0) # write adr 84 = 7 44 ac020054

```

The Verilog code is based off of the following images:

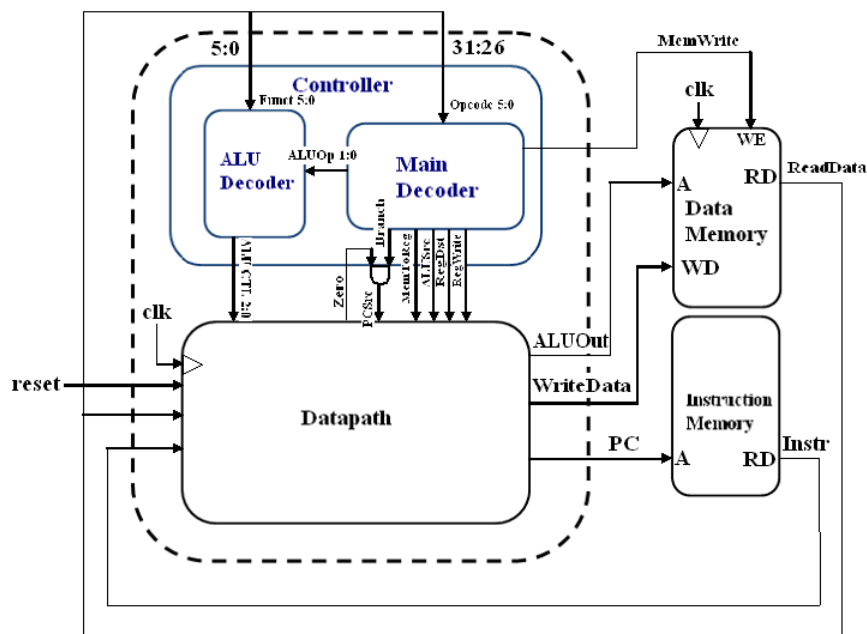


Figure 7: Single Cycle MIPS Processor

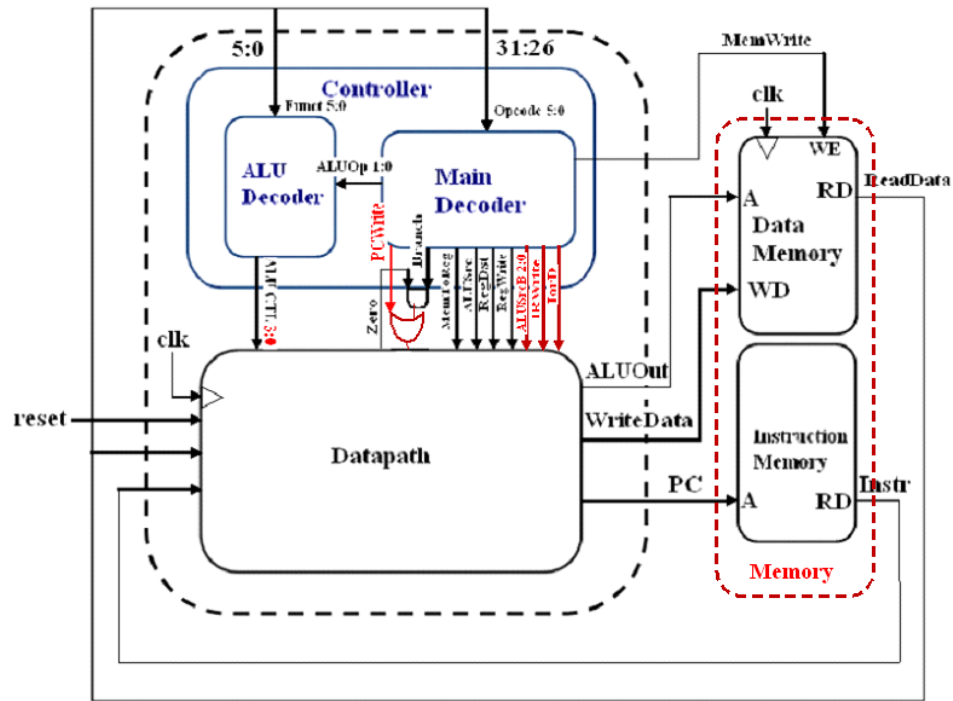


Figure 8: Multicycle MIPS Processor

Simulation

 


Figure 7: Simulation 0-70 ns

The simulation starts by asserting the “reset” signal to force the controller back to state 0 and clear any random data that appears during the turn on process. At 10 ns, the processor starts its first state 0 operation (fetch stage), where the instruction is retrieved from memory according to the Program Counter or PC. Once the instruction is fetched, the simulation enters the second state (decode stage) and the opcode appears. Depending on the opcode, the program chooses the next state. Since our simulation is for the addi instruction, state 9 will be the next state. The states for addi correspond to the FSM in Figure 3. As shown in Figure 3, state 10 will be the state after 9. State 9 and 10 occur at 30 and 40 ns respectively. Once these states are completed the controller returns to state 0 and the next instruction is fetched. However, the data has not been written back to the register designated by addi instruction. Looking at Figure 2, the data is stored in a clocked register during stage 10. When the controller enters state 0, the rising clock also triggers the register and puts it on the write data line of the register block. During the next clock cycle (60 ns), the data is then written to the register. As expected the length of the addi instruction is 4 cycles. However as shown above, the data may not be ready within that same time frame. This can be attributed to due to clock rate and registers that allow the multicycle MIPS processor to operate with the least amount of hardware.

Bibliography

Harris, David Money. Harris, Sarah L. Digital Design and Computer Architecture, San Francisco: Morgan Kaufman Publishers, 2007

Parhami, Behrooz. Computer Architecture, New York: Oxford University Press, 2005

Reference of Images

Figure 1: Parhami, Behrooz. Computer Architecture

Figure 2: Harris, David Money. Harris, Sarah L. Digital Design and Computer Architecture

Figure 5: Harris, David Money. Harris, Sarah L. Digital Design and Computer Architecture